

# Activity 4 – Analog v.s. Digital

We are going to control the speed of a small vibrating motor using analog values created with a potentiometer.

Digital		Analog	
A set number of values, such as ON and OFF.	ON	An infinite range of values	
	~		
	OFF		

## Potentiometer

A Potentiometer (pot) is a variable resistor. Turning the knob will increase or decrease the resistance between the middle pin and one of the outside pins.

By connecting the two outside pins of a potentiometer to 5V and GND, the middle pin will give us an **analog voltage value** between 5V and GND depending on how the knob is turned.

Circuit Diagram Symbol



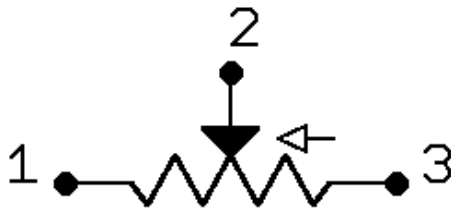


Image of Potentiometer on Breadboard<sup>1</sup>

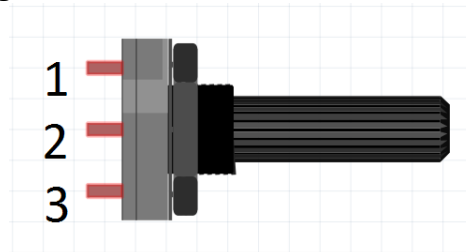

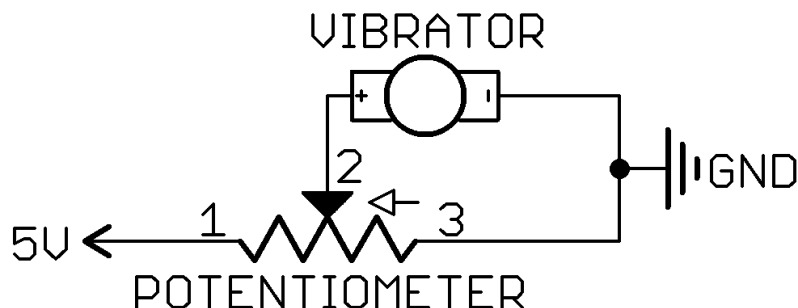
## Circuit Diagram to Control a Vibrator Using a Potentiometer







<sup>1</sup> Image from Fritzing

# Turning the Knob of the Potentiometer

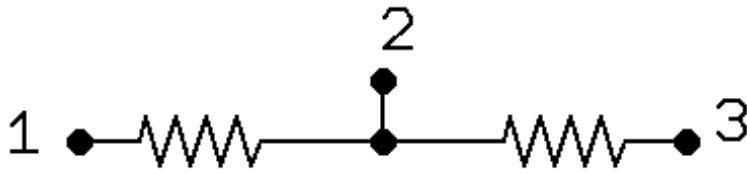

Knob centered.

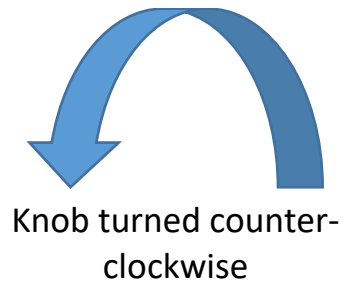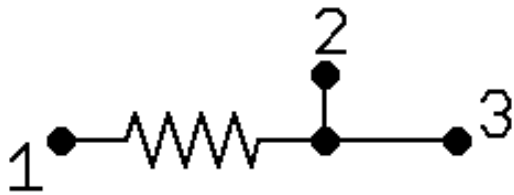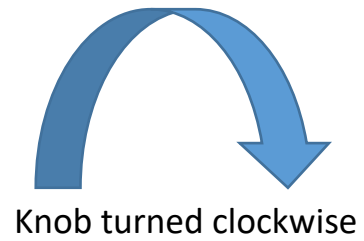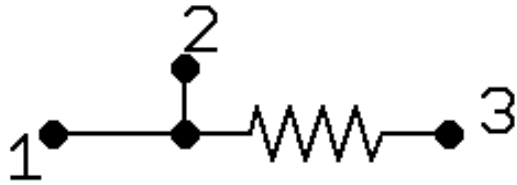

## Ideas, Observations, Questions